

# Analyzing a Circuit

(Prof. Matthew Newby,  
Temple University,  
Fall 2017)

① Break circuit into  $V + I$  regions




• all touching wires must be at same  $V$ .




• all straight segments must have same current, that is, current may only change at junctions.

Ex

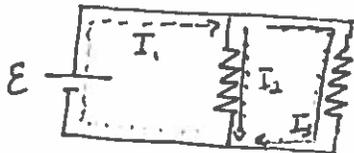

←  $+\epsilon = V$

←  $0 = V$

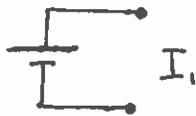


↑ 2 potentials  
← 3 currents

② Pick positive direction for currents

- like picking directional axes; positive currents in same direction as our "axis", negative in opposite direction.
- Pick a direction and stay consistent!
- Any direction will be fine.

● →  
ball moving, can pick  $+\hat{x}$   
to be either direction


Ex

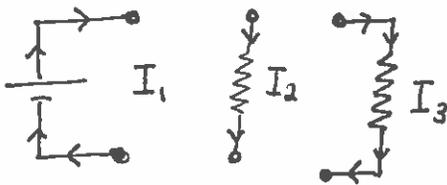

③ Kirchoff's Loop rule:  $\Delta V = 0$  around a loop

- Each circuit element encounter has a  $\Delta V_i$  associated with it. (Specifics later)

Ex

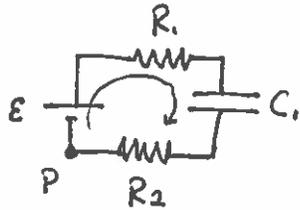

$$+\boxed{E} + \boxed{R_1} + \boxed{C_1} + \boxed{R_2} = 0$$


(Boxes represent terms)

- Pick a starting point ("p")
- Pick a direction & path around loop
- "Walk around loop, writing down a term whenever a component is encountered.
- When you get back to start ("p"), write "= 0" at the end.


④ Kirchoff's junction rule:  $I_{in} = I_{out}$  of a circuit junction

- Stick with the directions for current you picked earlier!

Ex

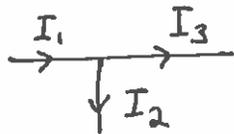

$$I_1 = I_2 + I_3$$

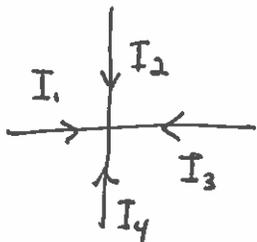


$$I_1 + I_2 + I_3 + I_4 = 0$$

We picked the  $\checkmark$  directions to all be into this junction. This is ok, at least one will be negative (unless all are zero)

— What to do for each circuit element?

- Keep  $I$  directions consistent with earlier!
- Let "----->" indicate the direction we are "walking" along a loop.

• Emf Source:

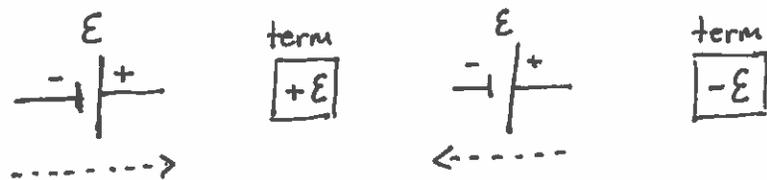

- We know the direction of (DC) emf, so the sign is whichever terminal we exit.
- For AC emfs, pick "+" to be the direction we chose for the current through that emf.


• Resistor:



- Encountering a resistor in the direction of the current assumes we are going "downhill"  $\Rightarrow \Delta V = -IR$
- Encountering a resistor in the opposite direction of the current implies the opposite: "uphill"  $\Delta V = -(-IR) = +IR$

For any resistor, we can always write:  $\Delta V = IR$

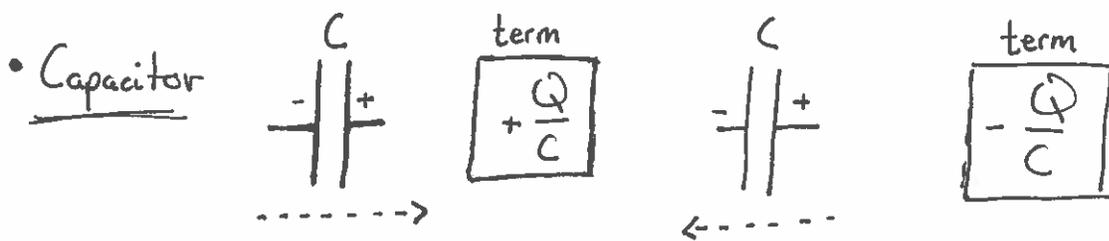
(For equivalent resistors,  $R \rightarrow R_{eq} \Rightarrow \Delta V = IR_{eq}$ )



- Capacitors are like emfs, need to know which side is "+"
- If we don't know, can write " $Q/C$ ";  $Q > 0$  implies charge aligns with our loop;  $Q < 0$  implies charge opposes loop.
- Current direction doesn't matter! (But it does determine if the capacitor is charging or discharging)

For any capacitor, we can always write:  $Q = CV$

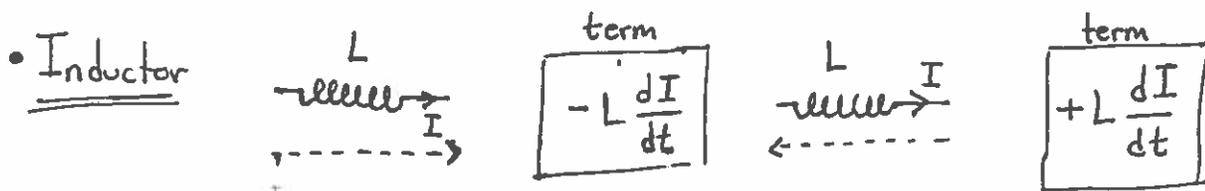(For equivalent capacitors,  $C \rightarrow C_{eq} \Rightarrow Q = C_{eq} V$ )



- Inductors oppose a changing current with a back emf.
- Sign is then relative to current direction.

For any inductor, can always write:  $\mathcal{E}_L = -L \frac{dI}{dt}$




- Diodes do not have a  $\Delta V$ , but instead dictate the allowed current direction: one way only!

⑤ Find equivalent components as needed.



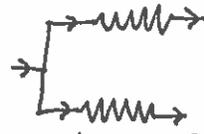- no choice for current  $\Rightarrow$  series
- equivalent components simplify sections of a circuit for easier analysis.



- choice for current  $\Rightarrow$  parallel

Note: May need to apply ③, ④, + ⑤ in different orders, depending on the circuit in question.


Note: Try to use loops + nodes that include the unknown(s) that you are solving for.

Note: You will need at least as many unique equations as unknowns.

Note: Knowns can often be simplified by replacing them with equivalent components.

Note: Playing around with a computerized circuit simulator will help you visualize how circuits work, without the need for an electronic store's supply of materials.


Example: Simple circuit

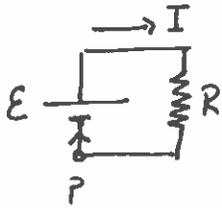

- I choose direction of I to be clockwise
- from p. loop:  $+ε - IR = 0$  (clockwise loop)

$$\Rightarrow ε = IR$$


Ex 2

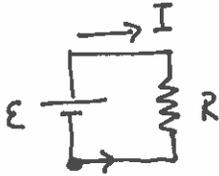

- I clockwise
- loop counter-clockwise

$$+IR - ε = 0 \Rightarrow ε = IR \quad \left( \begin{array}{l} \text{same} \\ \text{result!} \end{array} \right)$$


Ex 3 RLC w/ AC emf

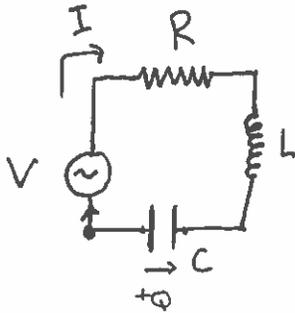


- I clockwise, loop will follow I
- loop:  $+V - IR - L \frac{dI}{dt} - \frac{Q}{C} = 0$

• Note: I defined "+Q" to be in the opposite direction of my current, this implies that it is being charged by the emf.



Ex 4

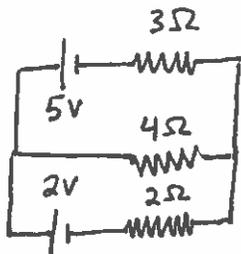


Find all three currents

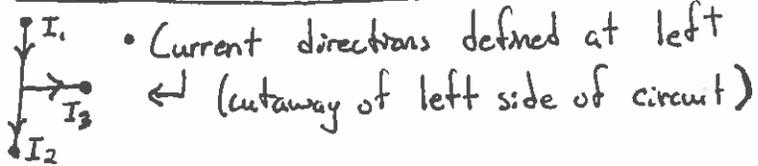

• Different currents:

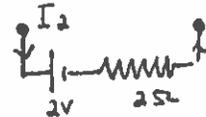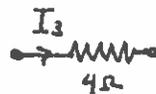

• Different potentials:

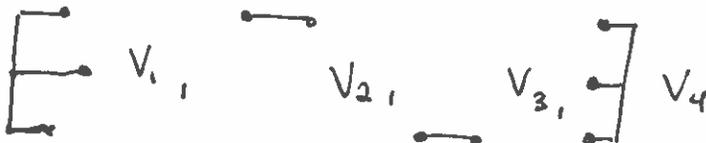

(continued)  
→

$\rightarrow$  junction rule:  $I_1 = I_2 + I_3$   
 top loop, counter-clockwise from 5V:  $+5V - 4I_3 - 3I_1 = 0$   
 bottom loop, clockwise from 2V:  $+2 - 4I_3 + 2I_2 = 0$   
 big loop, counter-clockwise from 5V:  $+5 - 2 - 2I_2 - 3I_1 = 0$

★

Rearranged:

- (i)  $5 = 3I_1 + 4I_3$
- (ii)  $2 = -2I_2 + 4I_3$
- (iii)  $3 = 3I_1 + 2I_2$

$\uparrow$  note:  
 with 3 unknowns,  
 we will only need  
 3 of these

junc. rule into (iii)  $\rightarrow 3 = 3(I_2 + I_3) + 2I_2 = 5I_2 + 3I_3$

solve (ii) for  $I_2 \rightarrow I_2 = 2I_3 - 1$

into iii again:  $\rightarrow 3 = 5(2I_3 - 1) + 3I_3$

$$3 = 10I_3 - 5 + 3I_3$$

$$8 = 13I_3$$

$$\Rightarrow \underline{\underline{I_3 = \frac{8}{13} A}}$$

into (ii)  $\rightarrow 2 = -2I_2 + 4\left(\frac{8}{13}\right)$


$$\Rightarrow \underline{\underline{I_2 = \frac{3}{13} A}}$$

Junc. rule:  $I_1 = I_2 + I_3 \Rightarrow \underline{\underline{I_1 = \frac{11}{13} A}}$

Note that we (accidentally) picked the correct directions for the currents, as they are all positive.

★ Just algebra from this point


Ex 5

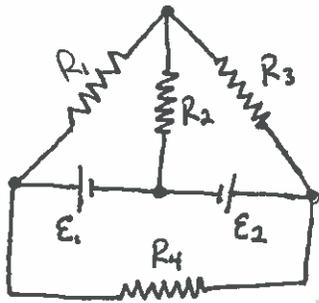

Find all currents

$$\begin{aligned} \mathcal{E}_1 &= \mathcal{E}_2 = 6V \\ R_1 &= R_3 = 3\Omega \\ R_2 &= 12\Omega \\ R_4 &= 10\Omega \end{aligned}$$

Redrawing:

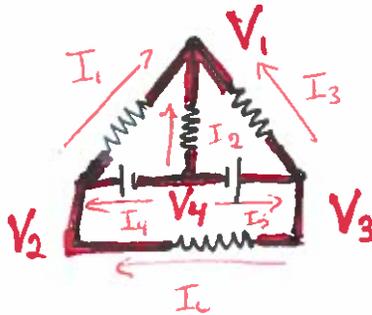

- 4 regions where potential can be different —
- 6 currents →

4 junctions:

$$\begin{aligned} I_1 + I_2 + I_3 &= 0 \\ I_4 + I_6 &= I_1 \\ 0 &= I_2 + I_4 + I_5 \\ I_5 &= I_6 + I_3 \end{aligned}$$

yikes!

→ 7 loops:



Start simple: bottom loop (□), clockwise from  $\mathcal{E}_2$ :

$$\begin{aligned} +\mathcal{E}_2 - I_6 R_4 - \mathcal{E}_1 &= 0 \Rightarrow (6V) - I_6(10\Omega) - (6V) = 0 \\ \Rightarrow \underline{\underline{I_6 = 0!}} & \quad (\text{potential is same on both sides of } R_4) \end{aligned}$$

This means (from junc. rules):  $I_1 = I_4$ ,  $I_3 = I_5$ ,  $\leftarrow$  eliminates  $I_4 + I_5$

Top-left loop ( $\Delta$ ); clockwise from  $\mathcal{E}_1$ :  $+\mathcal{E}_1 - I_1 R_1 + I_2 R_2 = 0$

Top-right loop ( $\Delta$ ); counter-clockwise from  $\mathcal{E}_2$ :  $+\mathcal{E}_2 - I_3 R_3 + I_2 R_2 = 0$

$\xrightarrow{\quad}$   
continued.

→ Rewriting what we have:

$$I_1 + I_2 + I_3 = 0, \quad I_1 = I_4, \quad I_3 = I_5, \quad I_6 = 0 \text{ A}$$

$$\mathcal{E}_1 - I_1 R_1 + I_2 R_2 = 0$$

$$\mathcal{E}_2 - I_3 R_3 + I_2 R_2 = 0$$

Now:  $\mathcal{E}_1 - I_1 R_1 + I_3 R_3 - \mathcal{E}_2 = 0$  (big triangle, )

$$\rightarrow (6\text{V}) - I_1(3\Omega) + I_3(3\Omega) - (6\text{V}) = 0$$

$$\rightarrow I_1(3\Omega) = I_3(3\Omega)$$

$$\Rightarrow I_1 = I_3 \quad \leftarrow \text{another current down}$$

junc. rule now gives:  $I_1 + I_2 + I_1 = 0 \Rightarrow 2I_1 = -I_2$

Into top-left loop ( $\Delta$ ):  $\mathcal{E}_1 - I_1 R_1 + (-2I_1) R_2 = 0$

$$\Rightarrow \mathcal{E}_1 - I_1(R_1 + 2R_2) = 0$$

$$\Rightarrow I_1 = \frac{\mathcal{E}_1}{R_1 + 2R_2} = \frac{6\text{V}}{(3\Omega) + 2(12\Omega)} = \frac{6\text{V}}{27\Omega} = \frac{2}{9} \text{ A}$$

Sol:  $I_1 = I_4 = \frac{2}{9} \text{ A}$

$$I_2 = -\frac{4}{9} \text{ A} \quad \leftarrow \text{picked opposite direction, here}$$

$$I_3 = I_5 = \frac{2}{9} \text{ A}$$

$$I_6 = 0 \text{ A}$$

Done! Not so bad?